



RULES:

1. Each component has its own symbol
2. Wires connect the components
3. Wires must be drawn with straight lines with a ruler
4. The wires should never cross each other